

M.E. 530.341 Lab 10: Analog to Digital and Digital to Analog Conversion

Noah J. Cowan*
Department of Mechanical Engineering
The Johns Hopkins University

Reading: Lecture notes
Spec sheet for ADC0831 8-Bit Serial Analog to Digital Converter IC.
Spec Sheet for TMP36GT9 analog temperature sensor IC.
BSII documentation for the SHIFTIN command (in BSII manual).
BSII Application Note 2: Using SHIFTIN and SHIFTOUT (in BSII manual).

Apparatus: ADC0831, TMP37GT9, Basic Stamp, Stamp Motherboard (Board of Education), AC Adapter, Basic Stamp development editor on a PC, RS232 cable, Oscilloscope,

1 Digital to Analog Conversion

Figure 1 shows the results of the circuit analysis we performed in class for the DAC circuit shown in Figure 1.

- 1) Choose two rows from Figure 1. Independently analyze the DAC circuit for these two cases to verify (or disprove) the results shown in the Figure 2.
- 2) Wire this simple D/A circuit, Figure 1, to I/O pins P12 through P15 on your breadboard. Use 1% resistors provided by your TA. We stock 1% resistors in 1K Ω , 2K Ω , and 4K Ω . Use two 4K Ω resistors to construct the 8K Ω resistor.

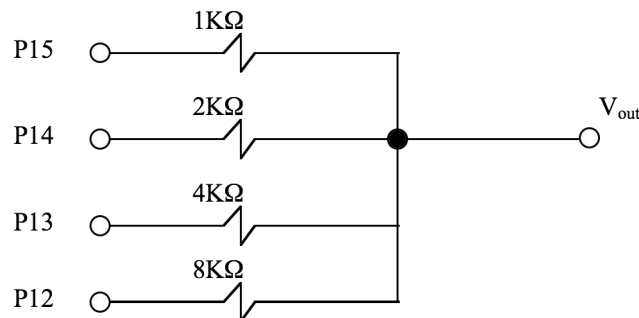


Figure 1: A Simple D/A Converter Circuit

- 3) Write a Stamp2 basic program to generate an ascending “ramp” of V_{out} voltage values – the output should begin at 0V and incrementally increase to 5V, then return to 0V.

* This laboratory © Louis L. Whitcomb. Updated with permission by Noah J. Cowan.


4) Use your scope to measure and print the waveform V_{out} . Title and annotate your plot.

P15	P14	P13	P12	R_L	R_H	R_L+R_H	$R_L/(R_L+R_H)$	V_{out}
0	0	0	0	533	∞	∞	0.000	0.00
0	0	0	1	571	8000	8571	0.067	0.33
0	0	1	0	615	4000	4615	0.133	0.67
0	0	1	1	666	2666	3333	0.200	1.00
0	1	0	0	727	2000	2727	0.267	1.33
0	1	0	1	800	1600	2400	0.333	1.67
0	1	1	0	888	1333	2222	0.400	2.00
0	1	1	1	1000	1142	2142	0.467	2.33
1	0	0	0	1142	1000	2142	0.533	2.67
1	0	0	1	1333	888	2222	0.600	3.00
1	0	1	0	1600	800	2400	0.667	3.33
1	0	1	1	2000	727	2727	0.733	3.67
1	1	0	0	2666	666	3333	0.800	4.00
1	1	0	1	4000	615	4615	0.867	4.33
1	1	1	0	8000	571	8571	0.933	4.67
1	1	1	1	∞	533	∞	1.000	5.00


Figure 2: DAC Output Table showing D/A output voltage as a function of P11-P15 logical (TTL) output.

2 Analog to Digital Conversion

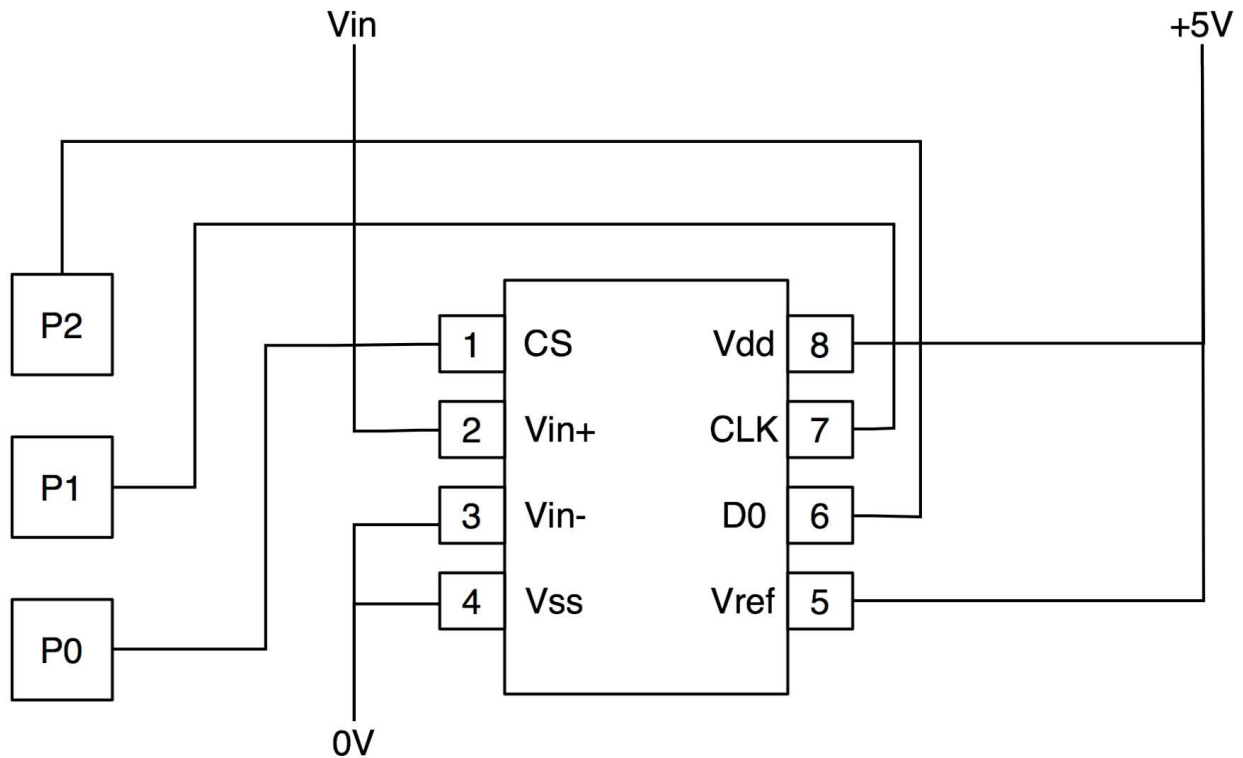- 5) Read the specification sheet for the ADC0831 Analog to Digital converter integrated circuit. Construct the following circuit:



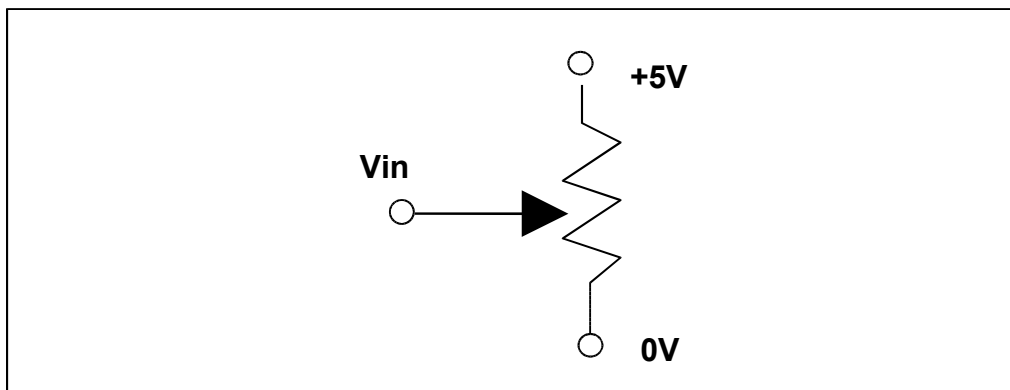- 6) Hook a potentiometer to the V_{in} signal to provide an adjustable voltage as shown below.



- 7) Write a program to use the ADC0831 to perform an analog-to-digital conversion of the voltage V_{in} , and to transfer the 8-bit digital value to the basic stamp. Your program should:
- Initialize by setting P2 (D0) to be an input,
 - Initialize P0 (CS) and P1 (CLK) to be outputs, with default values of HIGH and LOW.
 - To perform a conversion your program should:
 - Bring CS low to initiate A/D conversion
 - Read the A/D serial data with the SERIN command
 - Bring CS high to complete the conversion
 - Print out the A/D value

A sample program to read the A/D is as follows:

```
'{STAMP BS2}
' A/D Conversion with the ADC0831 Nov 3, 2003 LLW

' define variables
ad_byte var byte

' define constant labels for the 3 I/O pins
CS con 0
CLK con 1
D0 con 2

' configure CS line as output, quiescent state is high
OUTPUT CS
HIGH CS

' configure CLK line as output, quiescent state is low
OUTPUT CLK
LOW CLK

' top of sampling loop
TOP:

' a falling edge on CS initiates the A/D conversion
' and activates the D0 pin of the AD0831
low CS

' shift in the leading dummy bit and the 8 bits of A/D data
' data input on pin D0
' clock output on pin CLK
' A/D data is MSB first, loaded into variable AD_BYTE
shiftn D0, CLK, MSBPOST, [ad_byte\9]

' complete the conversion cycle and deactivate the D0 output
high cs

' print out the value of the A/D counts
debug "A/D count=", DEC ad_byte, CR


goto top
```

- 8) Hook a voltmeter to V_{in} . Hoop up your scope to display CLK on CH1 and D0 on CH2. Experiment with various settings of your potentiometer.
 - a) What is the A/D count value for $V_{in} = 0V$?
 - b) Repeat the above for $V_{in} = 2.5V$ or so.
 - c) Repeat the above for $V_{in} = 5.0V$.
- 9) Modify your program to display the A/D value in VOLTS or MILLIVOLTS.

3 Using the A/D with an Analog Temperature Sensor

This section is optional, it is not required.

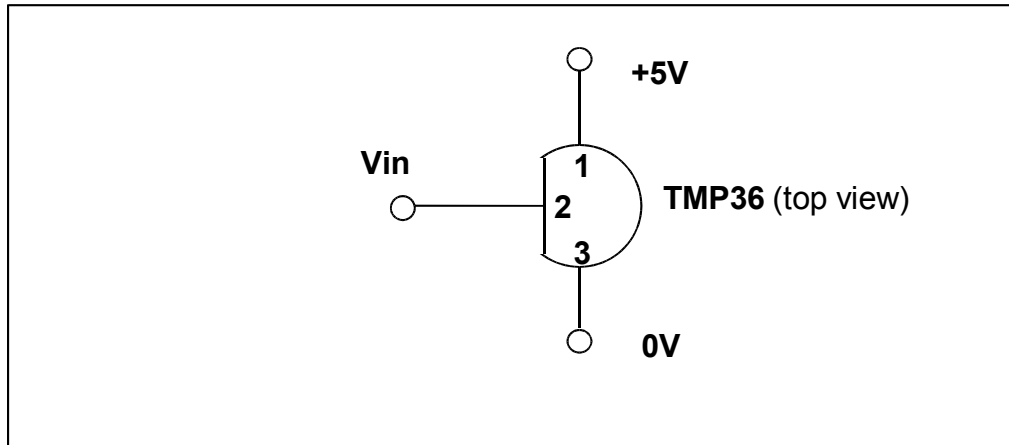10) Remove the potentiometer from your circuit and replace it with the TMP36 analog temperature sensor:



- 11) Read the spec sheet. What is the mathematical relationship between the temperature (in Celsius) and the output voltage (in volts)?
- 12) Write a program to read the output voltage of the TMP36 with the A/D converter, compute the temperature of in degrees Celsius, and print the temperature once a second. A sample program is given on the next page.
- 13) What happens when you warm up the temperature sensor by holding it in your fingers? When you let go?
- 14) Print a screen shot of the debug output while you are warming up the temperature sensor by holding it in your fingers.

-
- Hand in a floppy disk containing your programs with your lab. Floppy disks are available in the lab.
 - Remember to note your lab partner's name on your lab report.
 - Remember to show your work.
 - Typed or hand-written lab reports are OK. Messy or ambiguous lab reports will be rejected.
 - Please clean up your workstation to perfection when you are done.

```

'{$$STAMP BS2}
' A/D Conversion with the ADC0831 April 21, 2004 LLW
' define variables
ad_byte    VAR Byte
centivolts VAR Word
temp_C     VAR Word

' define constants as labels for the 3 I/O pins
CS  CON 0
CLK CON 1
D0  CON 2

' configure CS line as output, quiescent state is high
OUTPUT CS
HIGH  CS

' configure CLK line as output, quiescent state is low
OUTPUT CLK
LOW   CLK

' top of sampling loop

TOP:
' a falling edge on CS initiates the A/D conversion
' and activates the D0 pin of the AD0831

LOW CS
' shift in the leading dummy bit and the 8 bits of A/D data
' data input on pin D0
' clock output on pin CLK
' A/D data is MSB first, loaded into variable AD_BYTE

SHIFTIN D0, CLK, MSBPOST, [ad_byte\9]
' complete the conversion cycle and deactivate the D0 output
HIGH cs

' convert the A/D count to centivolts
centivolts = ad_byte * 500 /256

' compute temperature
' temp C = (volts - 0.5V) * 1 degree C / 1 centivolt
temp_C = (centivolts - 50)

' print out the value of the A/D counts

DEBUG "A/D Counts= ", DEC ad_byte
DEBUG " centivolts= ", DEC centivolts
DEBUG " Temp= ", DEC temp_C, " Centigrade"
DEBUG CR

PAUSE 1000 ' pause 1000 ms

GOTO top

```